

# Interactive Example Candidate Responses

## Paper 2 (May/June 2016), Question 7

### Cambridge International AS & A Level

### Physics 9702

In order to help us develop the highest quality resources, we are undertaking a continuous programme of review; not only to measure the success of our resources but also to highlight areas for improvement and to identify new development needs.

We invite you to complete our survey by visiting the website below. Your comments on the quality and relevance of our resources are very important to us.

[www.surveymonkey.co.uk/r/GL6ZNJB](http://www.surveymonkey.co.uk/r/GL6ZNJB)

Would you like to become a Cambridge International consultant and help us develop support materials?

Please follow the link below to register your interest.

[www.cambridgeinternational.org/cambridge-for/teachers/teacherconsultants/](http://www.cambridgeinternational.org/cambridge-for/teachers/teacherconsultants/)

Copyright © UCLES 2018

Cambridge Assessment International Education is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of the University of Cambridge Local Examinations Syndicate (UCLES), which itself is a department of the University of Cambridge.

UCLES retains the copyright on all its publications. Registered Centres are permitted to copy material from this booklet for their own internal use. However, we cannot give permission to Centres to photocopy any material that is acknowledged to a third party, even for internal use within a Centre.

- 7 (a) Electric current is a flow of charge carriers. The charge on the carriers is quantised. Explain what is meant by *quantised*.

*It means that charge is divide among the elations* [1]

- (b) A battery of electromotive force (e.m.f.) 9.0V and internal resistance 0.25Ω is connected in series with two identical resistors X and a resistor Y, as shown in Fig. 7.1.

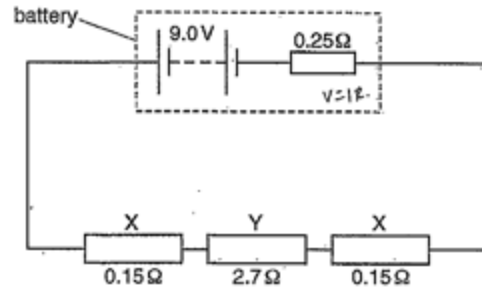


Fig. 7.1

The resistance of each resistor X is 0.15Ω and the resistance of resistor Y is 2.7Ω.

- (i) Show that the current in the circuit is 2.8A.

$$\frac{V_{\text{battery}}}{R_{\text{total}}} = I$$

$$I = \frac{9}{(0.25 + 0.15 + 0.15 + 2.7)}$$

$$= 2.769 \text{ A}$$

$$= 2.8 \text{ A}$$

[3]

- (ii) Calculate the potential difference across the battery.

$$V = IR$$

$$V = 2.8 \times 0.25$$

$$= 0.69$$

$$9 - 0.69$$

$$= 8.309$$

$$= 8.31$$

potential difference = 8.31 V [2]

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ <b>or</b> $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ <b>or</b> $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ <b>or</b> $8.4 \text{ V}$	C1 (C1) A1 [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) <b>or</b> resistance of Z goes up by 4x current goes down but by <u>less than</u> a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2] [Total: 10]

- (c) Each resistor X connected in the circuit in (b) is made from a wire with a cross-sectional area of  $2.5 \text{ mm}^2$ . The number of free electrons per unit volume in the wire is  $8.5 \times 10^{29} \text{ m}^{-3}$ .

- (i) Calculate the average drift speed of the electrons in X.

$$I = nAve$$

$$2.8 = 8.5 \times 10^{29} \times 2.5 \times 10^{-6} \times v \times 1.6 \times 10^{-19}$$

$$\frac{2.8}{3.4 \times 10^{17}} = v$$

$$v = 8.14 \times 10^{-12} \text{ m s}^{-1}$$

drift speed =  $8.14 \times 10^{-12} \text{ m s}^{-1}$  [2]

- (ii) The two resistors X are replaced by two resistors Z made of the same material and length but with half the diameter.

Describe and explain the difference between the average drift speed in Z and that in X.

Since the drift speed is inversely proportional to cross-sectional area, the drift speed in Z will be increased by 4 times. It will be four times more than X as the area is four times less than X.

[Total: 10]

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ or $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ or $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ or $8.4 \text{ V}$	C1 (C1) [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) or resistance of Z goes up by 4x current goes down but by less than a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2] [Total: 10]

- 7 (a) Electric current is a flow of charge carriers. The charge on the carriers is quantised. Explain what is meant by *quantised*.

'quantised' means expressed as a numerical value. [1]

- (b) A battery of electromotive force (e.m.f.) 9.0V and internal resistance 0.25Ω is connected in series with two identical resistors X and a resistor Y, as shown in Fig. 7.1.

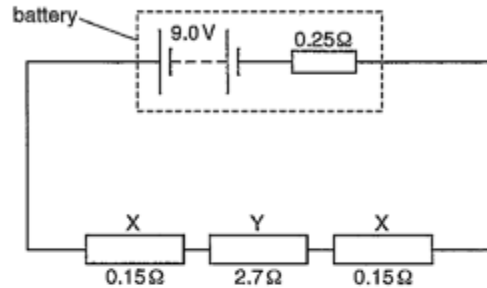


Fig. 7.1

The resistance of each resistor X is 0.15Ω and the resistance of resistor Y is 2.7Ω.

- (i) Show that the current in the circuit is 2.8A.

$$\begin{aligned} V &= IR \\ 9 &= I (0.25 + 0.15 + 0.15 + 2.7) \\ 9 &= I (3.25) \\ \therefore I &= 2.8 \text{ A} \quad \text{shown.} \end{aligned}$$

[3]

- (ii) Calculate the potential difference across the battery.

$$\begin{aligned} V &= IR \\ &= 2.8 \times 0.25 \\ &= 0.7 \text{ V} \end{aligned}$$

potential difference = 0.7 V [2]

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ or $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ or $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ or $8.4 \text{ V}$	C1 (C1) A1 [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) or resistance of Z goes up by 4x current goes down but by less than a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2]
		[Total: 10]

(c) Each resistor X connected in the circuit in (b) is made from a wire with a cross-sectional area of  $2.5 \text{ mm}^2$ . The number of free electrons per unit volume in the wire is  $8.5 \times 10^{29} \text{ m}^{-3}$ .

(i) Calculate the average drift speed of the electrons in X.

$$I = n A v q$$

$$2.8 = (8.5 \times 10^{29}) \cdot (2.5 \times 10^{-3}) \cdot (1.6 \times 10^{-19}) \cdot v$$

$$\therefore v = 8.2 \times 10^{-9} \text{ ms}^{-1}$$

$$\text{drift speed} = 8.2 \times 10^{-9} \text{ ms}^{-1} [2]$$

(ii) The two resistors X are replaced by two resistors Z made of the same material and length but with half the diameter.

Describe and explain the difference between the average drift speed in Z and that in X.

If the diameter is halved, the area is decreased by four times. According to  $I = n A v q$ , if the area decreases by four times, the ~~retard~~ average drift speed which increase by four times. [2]

[Total: 10]

$$\frac{I}{n A q} = v$$

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ <b>or</b> $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ <b>or</b> $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ <b>or</b> $8.4 \text{ V}$ A1	C1 (C1) [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) <b>or</b> resistance of Z goes up by 4x current goes down but by <u>less than</u> a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2] [Total: 10]

- 7 (a) Electric current is a flow of charge carriers. The charge on the carriers is quantised. Explain what is meant by *quantised*.

measured how many charge flows per unit time [1]

- (b) A battery of electromotive force (e.m.f.) 9.0 V and internal resistance 0.25  $\Omega$  is connected in series with two identical resistors X and a resistor Y, as shown in Fig. 7.1.

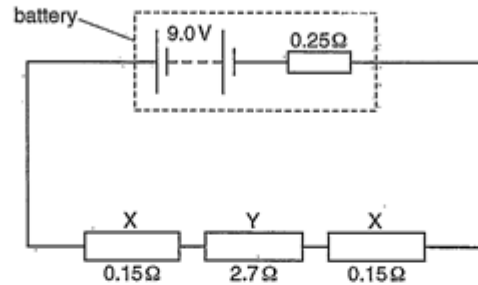


Fig. 7.1

The resistance of each resistor X is 0.15  $\Omega$  and the resistance of resistor Y is 2.7  $\Omega$ .

- (i) Show that the current in the circuit is 2.8 A.

$$\begin{aligned}
 E &= I(R + r + r + r) \\
 9.0 \text{ V} &= I(0.25 + 0.15 + 2.7 + 0.15) \\
 9.0 &= I(3.25) \\
 I &= \frac{9.0}{3.25} \\
 &= 2.769 \\
 &\approx 2.8 \text{ A}
 \end{aligned}$$

shown

[3]

- (ii) Calculate the potential difference across the battery.

$$\begin{aligned}
 V &= IR \\
 &= 2.769 \times 0.25 \\
 &= 0.692 \text{ V} \\
 &\approx 0.69 \text{ V}
 \end{aligned}$$

potential difference = 0.69 V [2]

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ <b>or</b> $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ <b>or</b> $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ <b>or</b> $8.4 \text{ V}$	C1 (C1) A1 [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) <b>or</b> resistance of Z goes up by 4x current goes down but by <u>less than</u> a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2]
		[Total: 10]

(c) Each resistor X connected in the circuit in (b) is made from a wire with a cross-section of  $2.5 \text{ mm}^2$ . The number of free electrons per unit volume in the wire is  $8.5 \times 10^{29} \text{ m}^{-3}$ .

$$2.5 \times 10^{-3} \text{ m}^2$$

(i) Calculate the average drift speed of the electrons in X.

$$I = nAve$$

$$2.8 = 8.5 \times 10^{29} \times 2.5 \times 10^{-3} \times v \times 1.60 \times 10^{-19}$$

$$2.8 = 3.4 \times 10^6 v$$

$$v = \frac{2.8}{3.4 \times 10^6}$$

$$v = 8.24 \times 10^{-7} \text{ drift speed} = 8.24 \times 10^{-7} \text{ m s}^{-1}$$

two resistors X are replaced by two resistors Z made of the same material but with half the diameter.

Describe and explain the difference between the average drift speed in Z and that in X.

Resistance is doubled therefore the current decreases. The average drift speed in Z is less than in X. This may be proved.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

Your  
Mark

7(a)

7(b)(i)

7(b)(ii)

7(c)(i)

7(c)(ii)

Q7	Mark scheme	
(a)	charge exists only in discrete amounts	B1 [1]
(b)(i)	$E = I(R + r)$ or $V = IR$ (total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ $I = 9.0 / (2.7 + 0.30 + 0.25)$ or $9.0 / 3.25 = 2.8 \text{ A}$	C1 M1 A1 [3]
(b)(ii)	$V = IR_{\text{ext}}$ $= 2.77 \times 3.0$ or $2.8 \times 3.0$ or $V = E - Ir$ $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$ $V = 8.3 (8.31) \text{ V}$ or $8.4 \text{ V}$	C1 (C1) A1 [2]
(c)(i)	$I = nevA$ $v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ $= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$	M1 A1 [2]
(c)(ii)	A reduces by a factor 4 (1/4 less) or resistance of Z goes up by 4x current goes down but by less than a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up	M1 A1 [2] [Total: 10]



Cambridge Assessment International Education  
The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA, United Kingdom  
t: +44 1223 553554 f: +44 1223 553558  
e: [info@cambridgeinternational.org](mailto:info@cambridgeinternational.org) [www.cambridgeinternational.org](http://www.cambridgeinternational.org)

Copyright © UCLES March 2018