

5: Electrical circuits – Topic questions

The questions in this document have been compiled from a number of past papers, as indicated in the table below.

Use these questions to formatively assess your learners' understanding of this topic.

Question	Year	Series	Paper number
6	2017	June	21
6	2017	March	22
7	2017	June	22

The mark scheme for each question is provided at the end of the document.

- 6 (a) Define the *ohm*.

.....
.....[1]

- (b) A cell X of electromotive force (e.m.f.) 1.5V and negligible internal resistance is connected in series to three resistors A, B and C, as shown in Fig. 6.1.

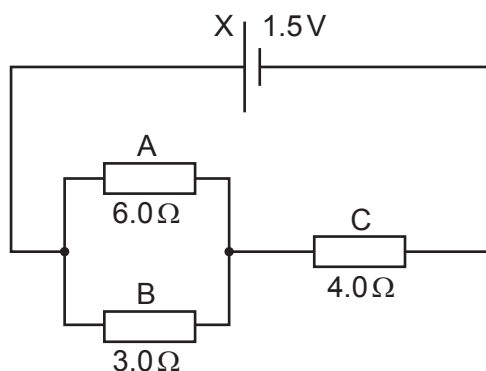


Fig. 6.1

Resistors A and B have resistances 6.0Ω and 3.0Ω respectively and are connected in parallel. Resistor C has resistance 4.0Ω and is connected in series with the parallel combination.

Calculate

- (i) the current in the circuit,

current =A [3]

- (ii) the current in resistor B,

current =A [1]

(iii) the ratio

$$\frac{\text{power dissipated in resistor B}}{\text{power dissipated in resistor C}}$$

ratio =[2]

(c) The resistors A, B and C in (b) are wires of the same material and have the same length.

(i) Explain how the resistors may be made with different resistance values.

.....[1]

(ii) Calculate the ratio

$$\frac{\text{average drift speed of the charge carriers in resistor B}}{\text{average drift speed of the charge carriers in resistor C}}$$

ratio =[2]

(d) A cell of e.m.f. 1.5V and negligible internal resistance is connected in parallel with cell X in Fig. 6.1 with their positive terminals together.

State the change, if any, to the current in

(i) cell X,

.....[1]

(ii) resistor C.

.....[1]

[Total: 12]

- 6 (a) Three resistors of resistances R_1 , R_2 and R_3 are connected as shown in Fig. 6.1.

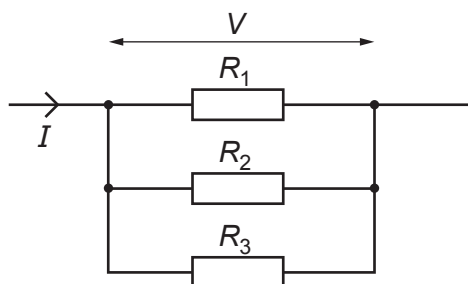


Fig. 6.1

The total current in the combination of resistors is I and the potential difference across the combination is V .

Show that the total resistance R of the combination is given by the equation

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$

[2]

- (b) A battery of electromotive force (e.m.f.) 6.0V and internal resistance r is connected to a resistor of resistance 12Ω and a variable resistor X , as shown in Fig. 6.2.

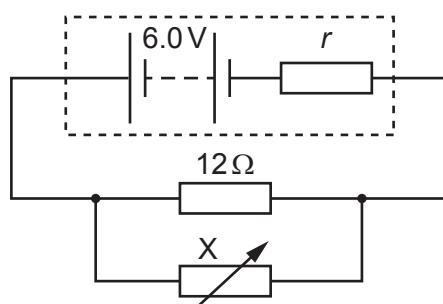


Fig. 6.2

- (i) By considering energy, explain why the potential difference across the battery's terminals is less than the e.m.f. of the battery.

.....

.....

.....

.....[2]

(ii) A charge of 2.5 kC passes through the battery.

Calculate

1. the total energy transformed by the battery,

energy = J [2]

2. the number of electrons that pass through the battery.

number = [1]

(iii) The combined resistance of the two resistors connected in parallel is 4.8Ω .

Calculate the resistance of X.

resistance of X = Ω [1]

(iv) Use your answer in (b)(iii) to determine the ratio

$$\frac{\text{power dissipated in X}}{\text{power dissipated in } 12\Omega \text{ resistor}}.$$

ratio = [2]

(v) The resistance of X is now decreased. Explain why the power produced by the battery is increased.

.....
.....
..... [1]

[Total: 11]

- 7 (a) Define *electromotive force* (e.m.f.) of a cell.

.....
[1]

- (b) A cell C of e.m.f. 1.50 V and internal resistance $0.200\ \Omega$ is connected in series with resistors X and Y, as shown in Fig. 7.1.

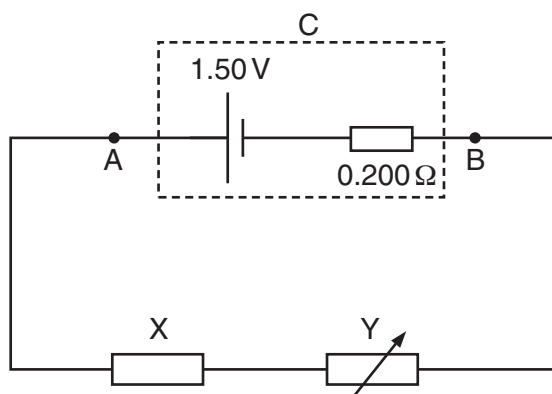


Fig. 7.1

The resistance of X is constant and the resistance of Y can be varied.

- (i) The resistance of Y is varied from 0 to $8.00\ \Omega$.

State and explain the variation in the potential difference (p.d.) between points A and B (terminal p.d. across C). Numerical values are not required.

.....

[3]

- (ii) The resistance of Y is set at $6.00\ \Omega$. The current in the circuit is 0.180 A.

Calculate

1. the resistance of X,

resistance = Ω [2]

2. the p.d. between points A and B,

p.d. = V [2]

3. the efficiency of the cell.

efficiency = [2]

[Total: 10]

Question	Answer	Marks
6 (a)	volt / ampere	1
6 (b) (i)	$R_T = [1 / 3.0 + 1 / 6.0]^{-1} + 4.0 (= 6.0 \Omega)$	1
	$I = 1.5 / 6.0$	1
	$= 0.25 \text{ A}$	1
6 (b) (ii)	$V_B = 0.5 \text{ V}$ $I = 0.5 / 3.0$ $= 0.17 (0.167) \text{ A}$	1
6 (b) (iii)	$P = I^2 R$ or VI or V^2 / R	1
	ratio $= (0.167^2 \times 3.0) / (0.25^2 \times 4.0)$ $= 0.33$	1
6 (c) (i)	vary/change/different radius/diameter/cross-sectional area (of wire)	1
6 (c) (ii)	$v = I / Ane$	1
	ratio $= \frac{(I_B/A_B)}{(I_C/A_C)}$ or $\frac{I_B}{I_C} \times \frac{A_C}{A_B}$ $(R \propto 1/A \text{ so})$ ratio $= \frac{I_B}{I_C} \times \frac{A_C}{A_B} = \frac{0.167}{0.25} \times \frac{3.0}{4.0}$ $= 0.50$	1
6 (d) (i)	0.25 A to 0.13 (0.125) A or halved	1
6 (d) (ii)	no change	1
Total: 12		
6 (a)	$I = I_1 + I_2 + I_3$	1
	$(V/R) = (V/R_1) + (V/R_2) + (V/R_3)$ or $(I/V) = (I_1/V) + (I_2/V) + (I_3/V)$ and (so) $1/R = 1/R_1 + 1/R_2 + 1/R_3$	1
6 (b) (i)	e.m.f. is total energy available per unit charge	1
	energy is dissipated in the internal resistance / resistor / r	1
6 (b) (ii) 1	Energy $= EQ$	1
	$= 6.0 \times 2.5 \times 10^3$ $= 1.5 \times 10^4 \text{ J}$	1
6 (b) (ii) 2	number $= 2.5 \times 10^3 / 1.6 \times 10^{-19}$ $= 1.6 \times 10^{22} (1.56 \times 10^{22})$	1
6 (b) (iii)	$1 / 4.8 = 1 / 12 + 1 / R_x$ $R_x = 8.0 \Omega$	1
6 (b) (iv)	$P = V^2 / R$ or $P = VI$ and $V = IR$	1
	ratio $= (V^2 / 8) / (V^2 / 12) = 12 / 8 = 1.5$	1
6 (b) (v)	(total) current, or I , increases and $P = EI$ or $P = 6I$ or $P \propto I$ or total (circuit) resistance decreases and $P = E^2/R$ or $P = 36/R$ or $P \propto 1/R$	1
Total: 11		

Question	Answer	Marks
7 (a)	energy transformed from chemical to electrical / unit charge (driven around a complete circuit)	1
7 (b) (i)	the current decreases (as resistance of Y increases)	1
	lost volts go down (as resistance of Y increases)	1
	p.d. AB increases (as resistance of Y increases)	1
7 (b) (i) 1	$1.50 = 0.180 \times (6.00 + 0.200 + R_x)$	1
	$R_x = 2.1(3) \Omega$	1
7 (b) (ii) 2	p.d. AB = $1.5 - (0.180 \times 0.200)$ or $0.18 \times (2.13 + 6.00)$	1
	= 1.46(4) V	1
7 (b) (ii) 3	efficiency = (useful) power output / (total) power input or IV / IE	1
	(= $1.46 / 1.5$) = 0.97 [0.98 if full figures used]	1
Total: 10		

Notes about the mark scheme are available separately.