



Interactive Example Candidate Responses

Paper 3 (May / June 2016), Question 10

Cambridge IGCSE™
Physics 0625



In order to help us develop the highest quality resources, we are undertaking a continuous programme of review; not only to measure the success of our resources but also to highlight areas for improvement and to identify new development needs.

We invite you to complete our survey by visiting the website below. Your comments on the quality and relevance of our resources are very important to us.

www.surveymonkey.co.uk/r/GL6ZNJB

Would you like to become a Cambridge International consultant and help us develop support materials?

Please follow the link below to register your interest.

www.cambridgeinternational.org/cambridge-for/teachers/teacherconsultants/

Copyright © UCLES 2017

Cambridge Assessment International Education is part of the Cambridge Assessment Group. Cambridge Assessment is the brand name of the University of Cambridge Local Examinations Syndicate (UCLES), which itself is a department of the University of Cambridge.

UCLES retains the copyright on all its publications. Registered Centres are permitted to copy material from this booklet for their own internal use. However, we cannot give permission to Centres to photocopy any material that is acknowledged to a third party, even for internal use within a Centre.

10 A student makes the circuit shown in Fig. 10.1 using a 12V battery.

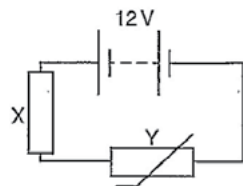


Fig. 10.1

(a) Complete the sentences about the circuit. Use words from the box.

fixed resistor lamp light-dependent resistor parallel series thermistor

(i) Components X and Y are connected in series [1]

(ii) The component Y is a fixed resistor [1]

(b) Fig. 10.2 shows how the resistance of Y varies with temperature.

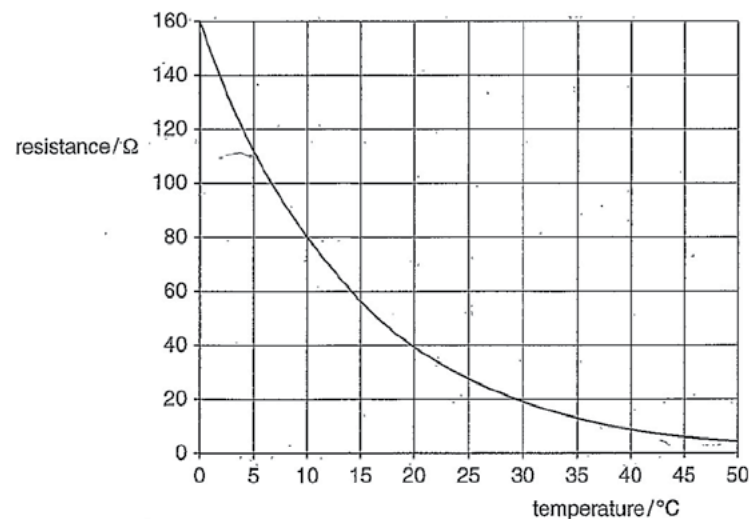


Fig. 10.2

(i) Describe how the resistance of Y varies with temperature.

The lesser the ^{temperature} resistance the
the higher the resistance
 [2]

Select
page

Your
Mark

10(a)(i)

10(a)(ii)

10(b)(i)

10(b)(ii)

10(b)(iii)

Q10	Mark scheme
(a)(i)	<u>series</u>
(a)(ii)	<u>thermistor</u>
(b)(i)	resistance decreases as temp increases at decreasing rate OR not proportional OR not linear
(b)(ii)	resistance of Y = 80 Ω $R_t = R_1 + R_2$ in any form 100 (Ω)
(b)(iii)	$V = IR$ in any form 12 ÷ 100 OR 12 ÷ candidates (b)(ii) 0.12 (A) OR ECF from (b)(ii)

(ii) The temperature of Y is 10°C . The resistance of X is 20Ω .

Calculate the combined resistance of Y and X.

$$\frac{80 \times 20}{100} = 16$$

resistance = 100 Ω [3]

(iii) Calculate the current in the circuit.

$$I = \frac{V}{R}$$

$$\frac{12}{100}$$

current = 0.12 A [3]

[Total: 10]

$$I = 12$$

$$160 + 140 + 120 + 100 + 80 + 60 + 40 + 20 = 720$$

Your
Mark

10(a)(i)

10(a)(ii)

10(b)(i)

10(b)(ii)

10(b)(iii)

Q10	Mark scheme
(a)(i)	<u>series</u>
(a)(ii)	<u>thermistor</u>
(b)(i)	resistance decreases as temp increases at decreasing rate OR not proportional OR not linear
(b)(ii)	resistance of Y = 80Ω $R_t = R_1 + R_2$ in any form $100(\Omega)$
(b)(iii)	$V = IR$ in any form $12 \div 100$ OR $12 \div$ candidates (b)(ii) 0.12 (A) OR ECF from (b)(ii)

10 A student makes the circuit shown in Fig. 10.1 using a 12V battery.

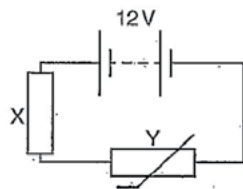


Fig. 10.1

(a) Complete the sentences about the circuit. Use words from the box.

fixed resistor lamp light-dependent resistor parallel series thermistor

(i) Components X and Y are connected in parallel [1]

(ii) The component Y is a fixed resistor. [1]

(b) Fig. 10.2 shows how the resistance of Y varies with temperature.

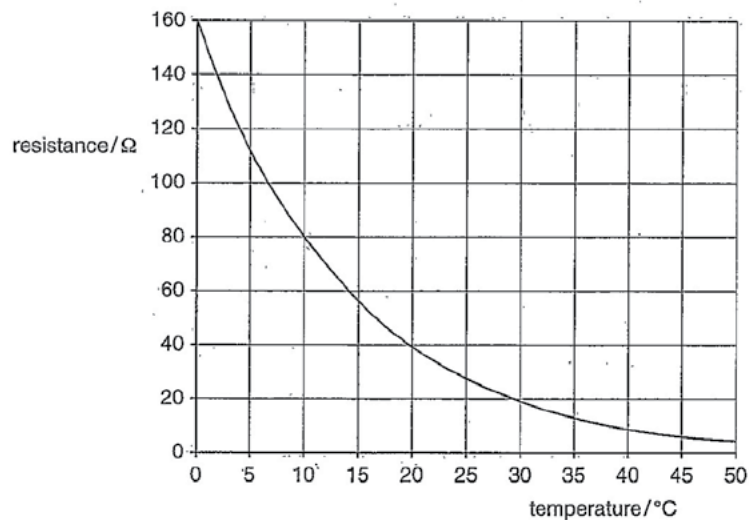


Fig. 10.2

(i) Describe how the resistance of Y varies with temperature.

As the resistance of y decreases the
temperature of y increases.
 [2]

Select
page

Your
Mark

10(a)(i)

10(a)(ii)

10(b)(i)

10(b)(ii)

10(b)(iii)

Q10	Mark scheme
(a)(i)	<u>series</u>
(a)(ii)	<u>thermistor</u>
(b)(i)	resistance decreases as temp increases at decreasing rate OR not proportional OR not linear
(b)(ii)	resistance of Y = 80 Ω $R_t = R_1 + R_2$ in any form 100 (Ω)
(b)(iii)	$V = IR$ in any form 12 ÷ 100 OR 12 ÷ candidates (b)(ii) 0.12 (A) OR ECF from (b)(ii)

(ii) The temperature of Y is 10°C. The resistance of X is 20Ω.

Calculate the combined resistance of Y and X.

$$r = R_1 \times R_2$$

$$r = 80\Omega \times 20\Omega = 1600\Omega$$

resistance = 1600 Ω [3]

(iii) Calculate the current in the circuit.

$$\text{Current} = \frac{V}{R} = \frac{1600\Omega}{12V} = 133.3A$$

current = 133.3 A [3]

[Total: 10]

Your
Mark

10(a)(i)

10(a)(ii)

10(b)(i)

10(b)(ii)

10(b)(iii)

Q10	Mark scheme
(a)(i)	<u>series</u>
(a)(ii)	<u>thermistor</u>
(b)(i)	resistance decreases as temp increases at decreasing rate OR not proportional OR not linear
(b)(ii)	resistance of Y = 80Ω $R_t = R_1 + R_2$ in any form 100 (Ω)
(b)(iii)	$V = IR$ in any form 12 ÷ 100 OR 12 ÷ candidates (b)(ii) 0.12 (A) OR ECF from (b)(ii)

Cambridge Assessment International Education
The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA, United Kingdom
t: +44 1223 553554
e: info@cambridgeinternational.org www.cambridgeinternational.org

Copyright © UCLES September 2017